

## **Circuit Theory and Electronics Fundamentals**

### **Lab 3 - AC/DC Converter**

### **Aerospace Engineering**

Laboratory Report

May 8, 2021

Eva Claro, 95785

Miguel Isidoro, 95834

Pedro Braz, 95837

# Contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>4</b>
2.1	Natural Solution with node analysis for $t \geq 0$ . . . . .	4
2.2	Natural and Forced Superimposed . . . . .	4
<b>3</b>	<b>Simulation Analysis</b>	<b>6</b>
<b>4</b>	<b>Conclusion</b>	<b>12</b>

# 1 Introduction

This report is being made for the subject of Circuit Theory and Electronics Fundamentals and is related to the third laboratory being its objective to develop an AC/DC converter circuit using an envelope detector and a voltage regulator. The display of this circuit can be seen in Figure 1. In Section 2 a theoretical analysis will be made. Secondly, in Section 3 it will be simulated the circuit using ngspice. Following with both results from Section 2 and Section 3 being compared and commented in Section ??

The conclusions of this study are outlined in Section 4.

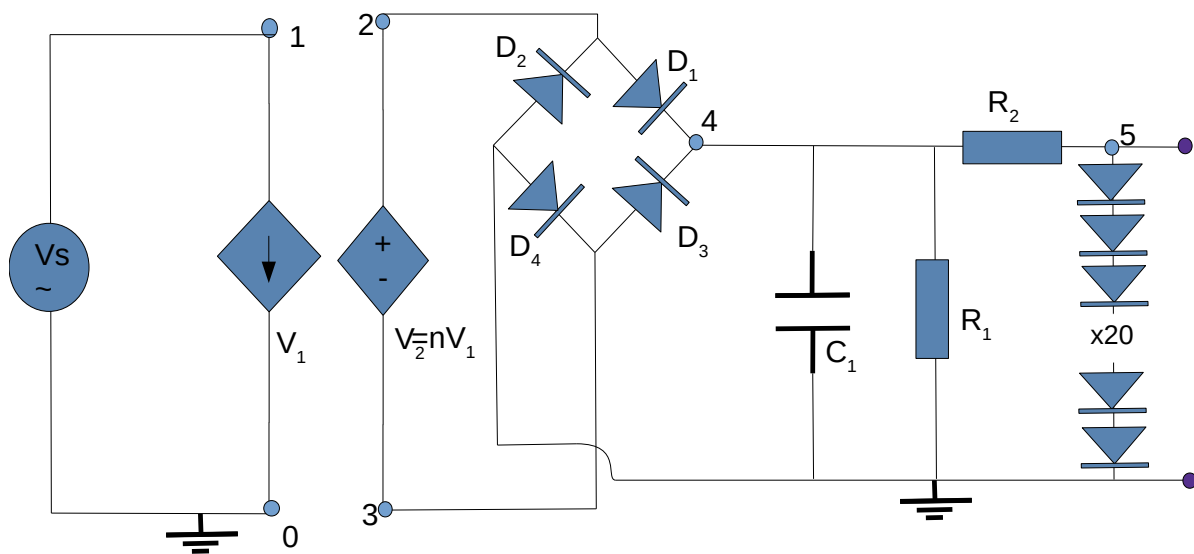


Figure 1: AC/DC converter circuit

## 2 Theoretical Analysis

In this section, the output voltage, voltage ripple and envelope detector output of the circuit shown in Figure 1 will be analysed theoretical.

### 2.1 Natural Solution with node analysis for $t \geq 0$

The aim of this section is to calculate the natural solution of  $v_{6n}(t)$ . Hence, the graph of  $V_{6n}$  in function of the time, in the interval  $[0;20]$  ms is represent in 2. The result is no surprise, as it shows below, being a negative exponential graph.

 


Figure 2: Deflection from the wanted DC voltage

### 2.2 Natural and Forced Superimposed

In this subsection, we determine the final total solution for the value of  $v_6$  for the given

In Figure 3 we plotted the graphs of  $v_6(t)$  and  $v_s(t)$  in the interval  $[-5;20]$  ms. We can clearly divide the solutions in three parts:

 


Figure 3: Output voltage of the regulator

 


Figure 4: Output voltage of the envelope

 


Figure 5: Output voltage of the rectifier regulator and the envelope

### 3 Simulation Analysis

This section covers the circuit simulation using the Ngspice tool, where the AC/DC converter was simulated for 10 periods using the default diode model.

Firstly, the transformer was replaced by an ideal model using an dependent current source and an dependent voltage source. Then, by trial and error the values of the resistors, capacitor and n parameter were adjusted reaching a good accuracy. The goal was to reach the closest value to 12V in the output voltage.

As asked in the lab assignment, the input voltage of the the secondary circuit, the output voltage of the envelope detector, the output voltage of the voltage regulator and (v(5)-12) were computed and plotted.

Later in this report, we will compare this results with the theoretical ones but for now we will just show them.

 


Figure 6: AC/DC converter circuit

The Table 1 shows the output voltages results for the circuit described in Figure 6.

Name	Value [A or V]
maximum(v(4))-minimum(v(4))	7.243825e-01
mean(v(4))	1.256325e+01
maximum(v(5))-minimum(v(5))	3.427691e-01
mean(v(5))	1.196956e+01

Table 1: Output voltages results in Volts

The Table 2 show the merit value obtained by the group.

Name	Value [A or V]
1/(((maximum(v(5))-minimum(v(5)))*(mean(v(5)))+10e-6)	2.437356e-01

Table 2: Merit values

 


Figure 7: Output Voltage of the envelope detector v(4)

 


Figure 8: Input Voltage of the secondary circuit (v(2)-v(3))



 


Figure 9: Output Voltage of the voltage regulator v(5)

 


Figure 10: Simulated voltage output error (v(5)-12)

 


Figure 11: Total Response of  $V_6$  and  $V_s$

## **4 Conclusion**

The objective of this laboratory assignment was to develop an AC/DC converter circuit and that goal was achieved. The error was The merit was So we can conclude that the circuit created was...